

DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE

Regular & Supplementary Winter Examination-2023

Course: B. Tech.

Semester III

Branch : Electronics Engineering/Electronics and Telecommunication

Engineering/Electronics and Communication Engineering

Subject Code & Name: BTEXC302/BTETC302 and Electronic Devices and Circuits

Max Marks: 60

Date:04-01-2024

Duration: 3 Hr.

Instructions to the Students:

1. All the questions are compulsory.
2. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in ( ) in front of the question.
3. Use of non-programmable scientific calculators is allowed.
4. Assume suitable data wherever necessary and mention it clearly.

(Level/CO) Marks

Q.1 Solve Any Two of the following.

12

- A) Draw a neat circuit diagram of CB connection. Define  $\alpha$ . Find the expression for collector current. CO3 6
- B) Explain transistor as an amplifier in CE configuration. CO3 6
- C) Determine  $V_{CB}$  in the transistor circuit shown in figure (a). The transistor is silicon and has  $\beta = 150$ . CO2/CO3 6

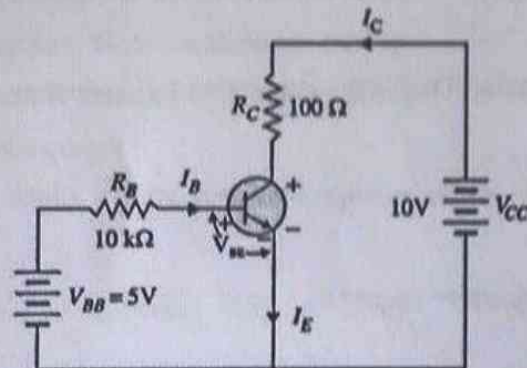


Figure (a)

Q.2 Solve Any Two of the following.

12

- A) With a neat diagram, explain the working principle of p-channel D-MOSFET with different cases. CO2/CO3 6
- B) Give the comparison of FET with MOSFET and BJT. CO3 6
- C) A JFET has a drain current of 5mA. If  $I_{DSS} = 10\text{mA}$  and  $V_{GS(off)} = -6\text{V}$ , find the value of (i)  $V_{GS}$  and (ii)  $V_P$ . CO3 6

- Co  
Ma
- Q. 3 Solve Any Two of the following.** 12
- A) Discuss with neat diagram transformer coupled class A power amplifier and derive its maximum efficiency. CO2/CO4 6
- B) Prove that the maximum conversion efficiency of a Class B transformer coupled amplifier is 78.5%. CO2/CO4 6
- C) With a neat diagram explain push-pull class B power amplifier and derive its maximum efficiency. CO1/CO4 6
- Q.4 Solve Any Two of the following.** 12
- A) Explain voltage series feedback amplifier with a neat diagram. How the overall gain, input impedance, output impedance is affected in these amplifiers. CO4 6
- B) Explain current series feedback amplifier with a neat diagram. How the input impedance, output impedance are affected in these amplifiers. CO2/CO4 6
- C) State and explain Barkhausen criterion of oscillations. CO4 6
- Q. 5 Solve Any Two of the following.** 12
- A) Draw and explain the Wein Bridge oscillator. Derive the expression for frequency of oscillation. CO2/CO4 6
- B) Draw and explain the Hartley oscillator. Derive the expression for frequency of oscillation. CO2/CO4 6
- C) Define voltage regulation. Explain series voltage regulator with a block diagram. CO4 6

\*\*\* End \*\*\*